

## Tutorial Problem Sheet 2

**Question 1.** An ideal op-amp circuit is given in Figure 1

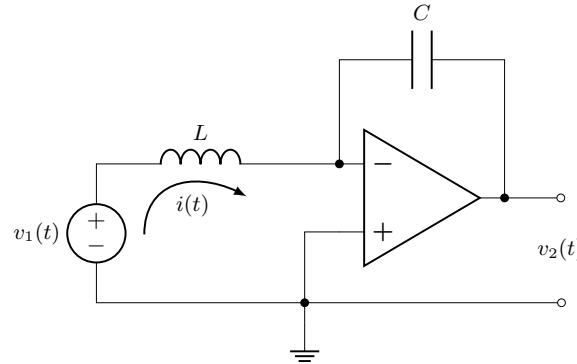


Figure 1

where  $i(t)$  is the current,  $v_1(t)$  is the input and  $v_2(t)$  is the output.

- Derive the state space model for the circuit in Figure 1 using the state variables  $x_1 = i(t)$  and  $x_2 = v_2(t)$ .
- Using your answer from part (a), obtain the transfer function  $G(s)$  of the circuit in Figure 1.
- Find the state transition matrix  $e^{At}$  such that  $\mathbf{x}(t) = e^{At}\mathbf{x}(0)$ .
- Find the equilibrium point of the circuit in Figure 1.

**Question 2.** Consider the discrete-time linear system

$$\begin{aligned}\mathbf{x}[k+1] &= \mathbf{A}\mathbf{x}[k] + \mathbf{B}u[k], \\ y[k] &= \mathbf{C}\mathbf{x}[k],\end{aligned}$$

where

$$\mathbf{A} = \begin{bmatrix} 1 & 0 \\ -\frac{T}{C} & 1 \end{bmatrix}, \quad \mathbf{B} = \begin{bmatrix} \frac{T}{L} \\ 0 \end{bmatrix}, \quad \mathbf{C} = \begin{bmatrix} 0 & 1 \end{bmatrix},$$

and  $T > 0$  is the sampling period.

- Show that the discrete-time state matrix  $\mathbf{A}$  corresponds to the continuous-time system studied in Question 1.
- Compute  $\mathbf{A}^k$  for all  $k \geq 0$ .
- Hence, derive an explicit expression for the state trajectory  $\mathbf{x}[k]$  in terms of the initial condition  $\mathbf{x}[0]$  and the input sequence  $\{u[0], u[1], \dots, u[k-1]\}$ .
- Assume  $u[k] = 0$  for all  $k$ . Describe the free response of the system.
- Determine all equilibrium points of the discrete-time system and compare them with the equilibrium points of the continuous-time model.